

# Basics of Electronics

Electronics Circuit

Terminology


Components

Basic Circuit with Arduino



# Electronic Circuit

- Electronic components, connected by wire through which electric current can flow
- Needs three components: source, connection, consumer
- Specific laws, symbols and terminology


# Simple Circuit

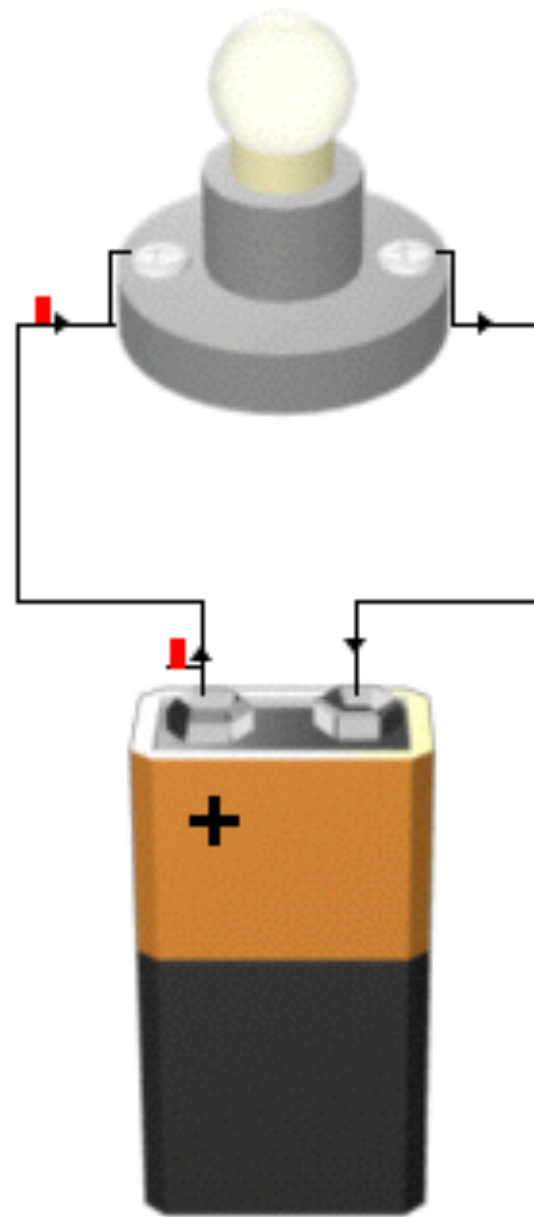


# Simple Circuit

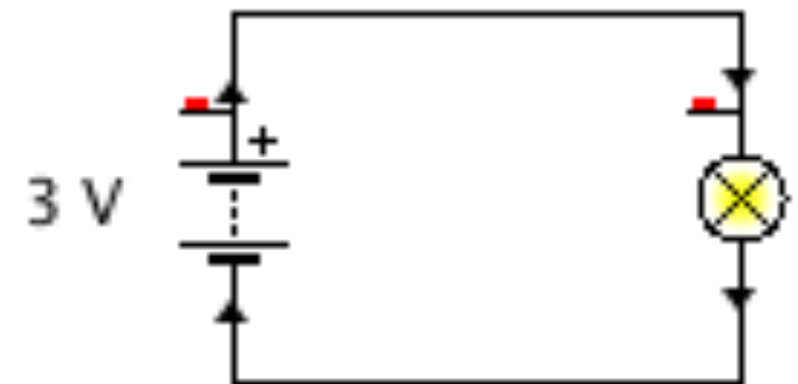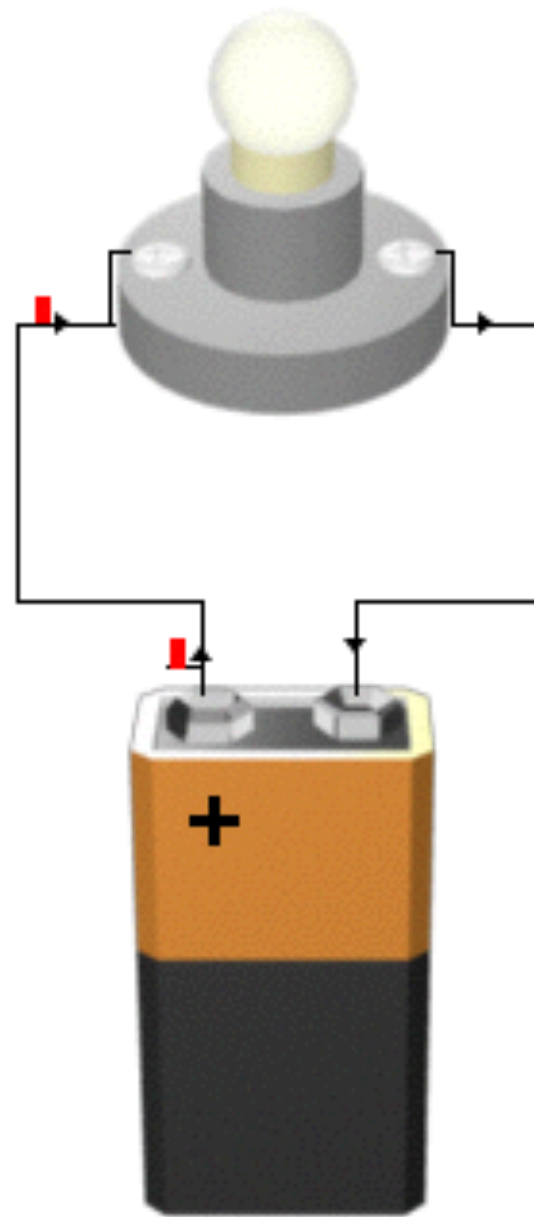


# Simple Circuit 2

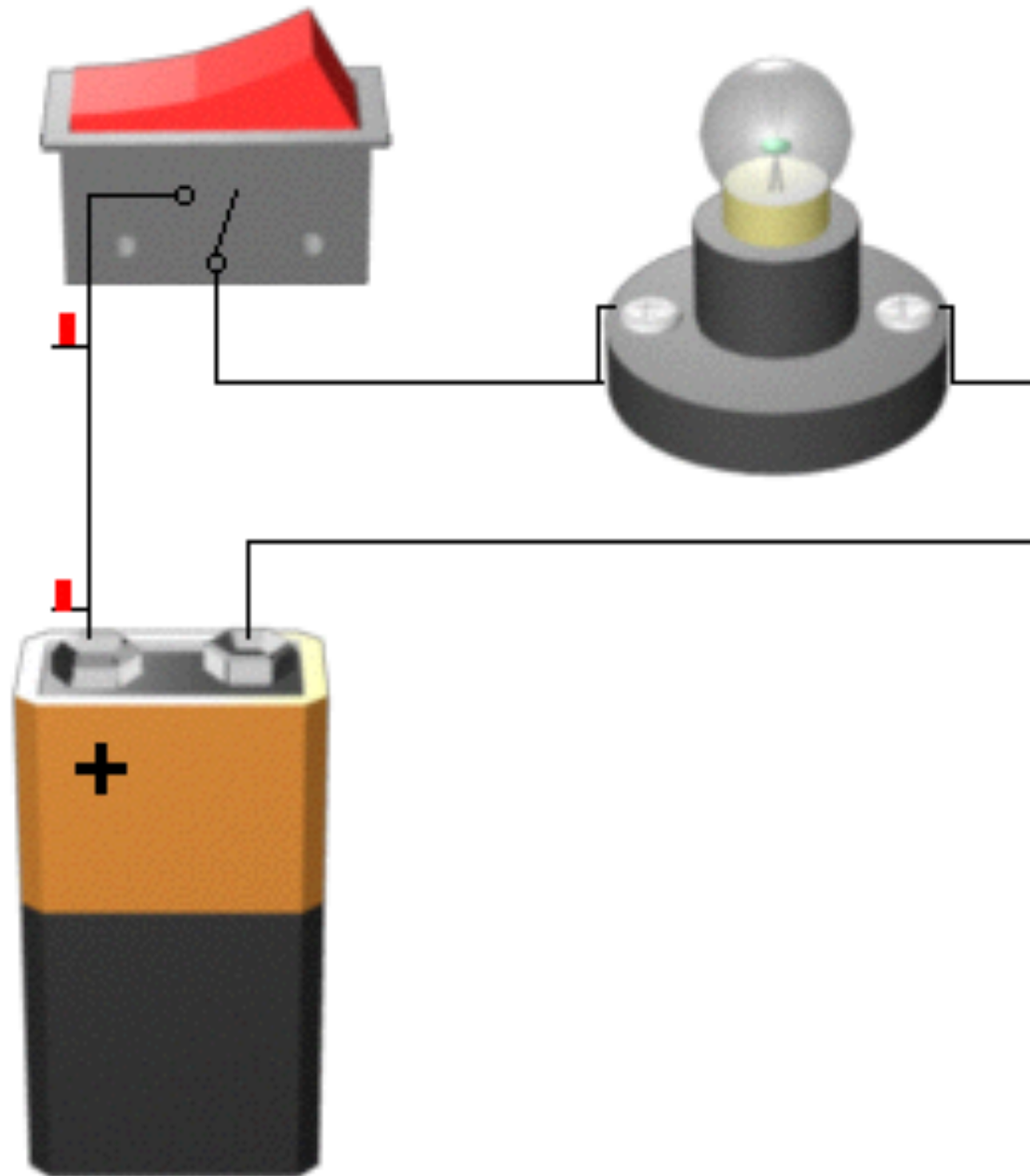


# Simple Circuit 2

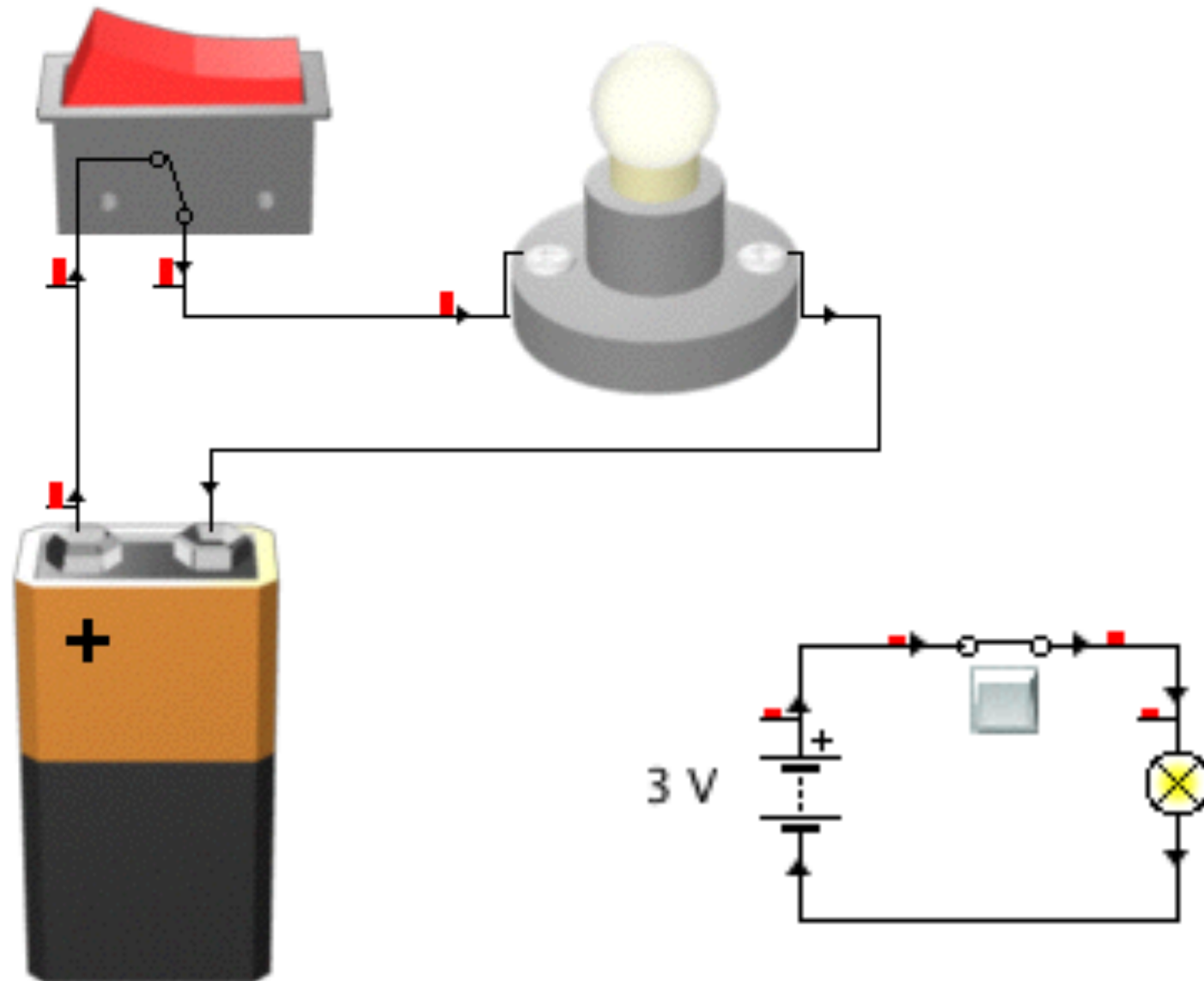

# Series Circuit

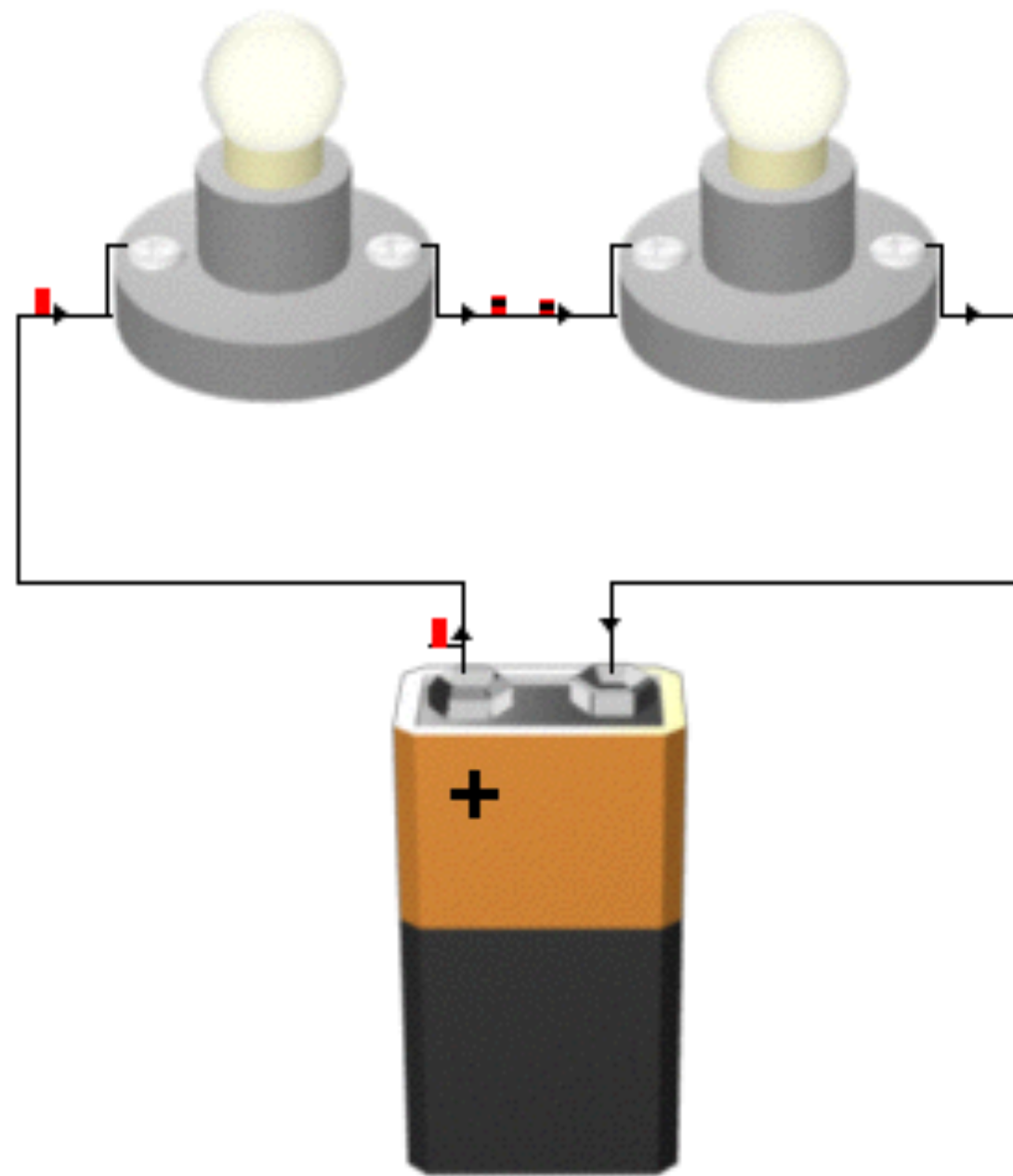


# Parallel Circuit

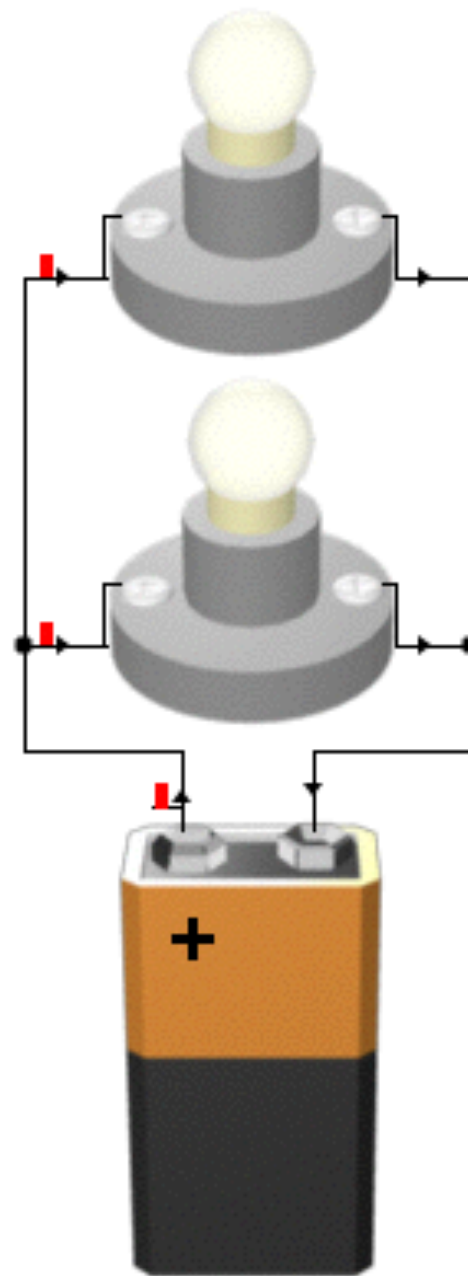





# Circuits

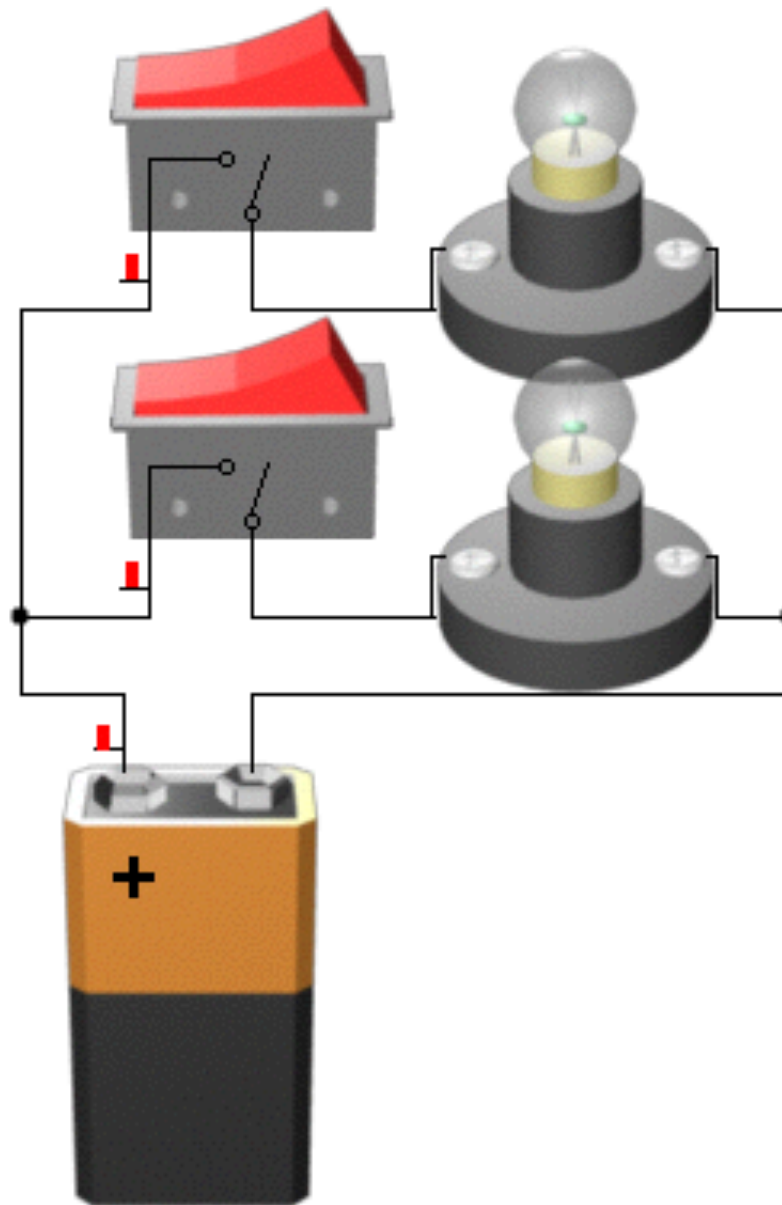

# Circuits

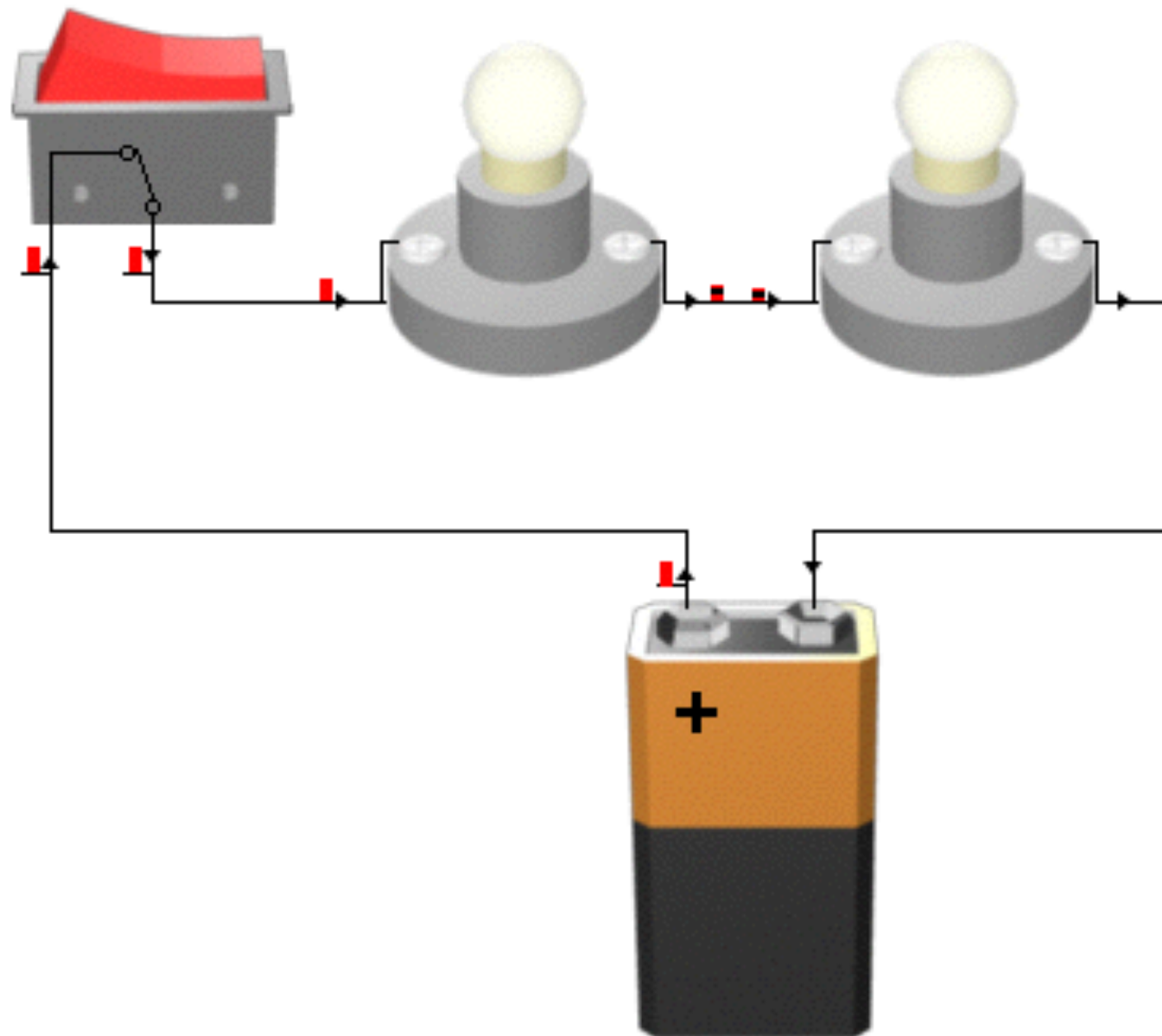

# Circuits

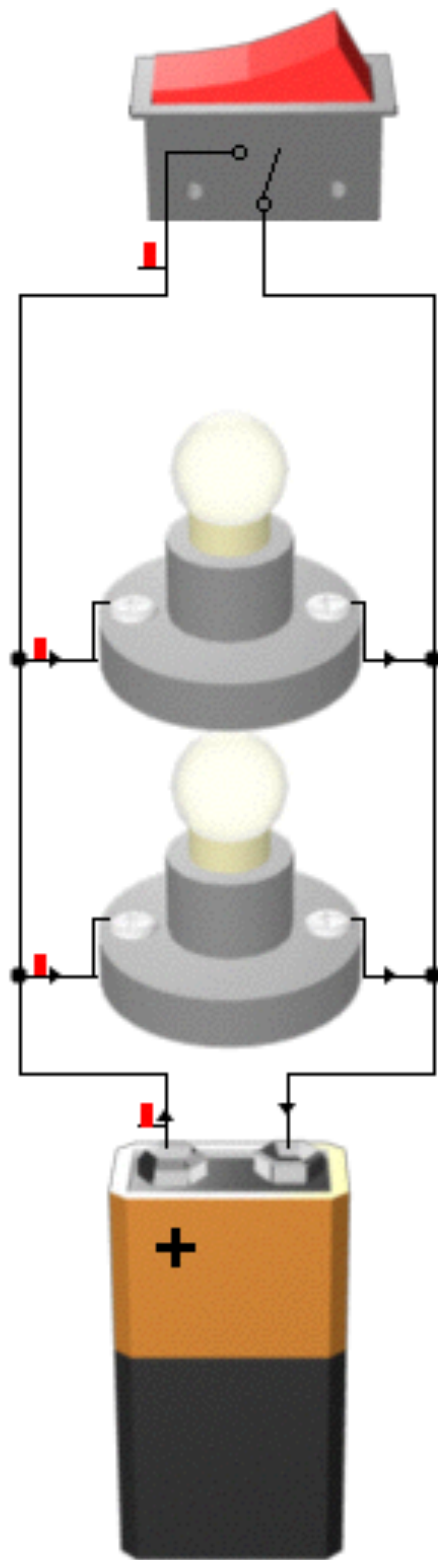


# Circuits

Never create something like this!

short circuit

-> electronic circuit with no consumer

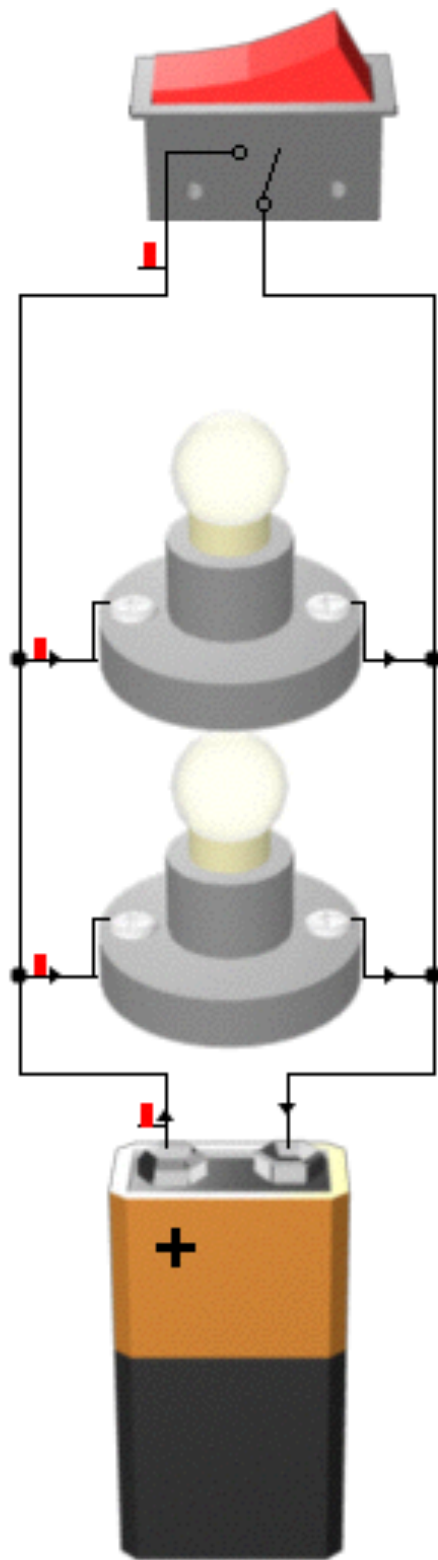

# Ohm's Law

$$U = R * I$$

U = Voltage in Volt, R = Resistance in  $\Omega$ , I = Current in Ampere

# Ohm's Law



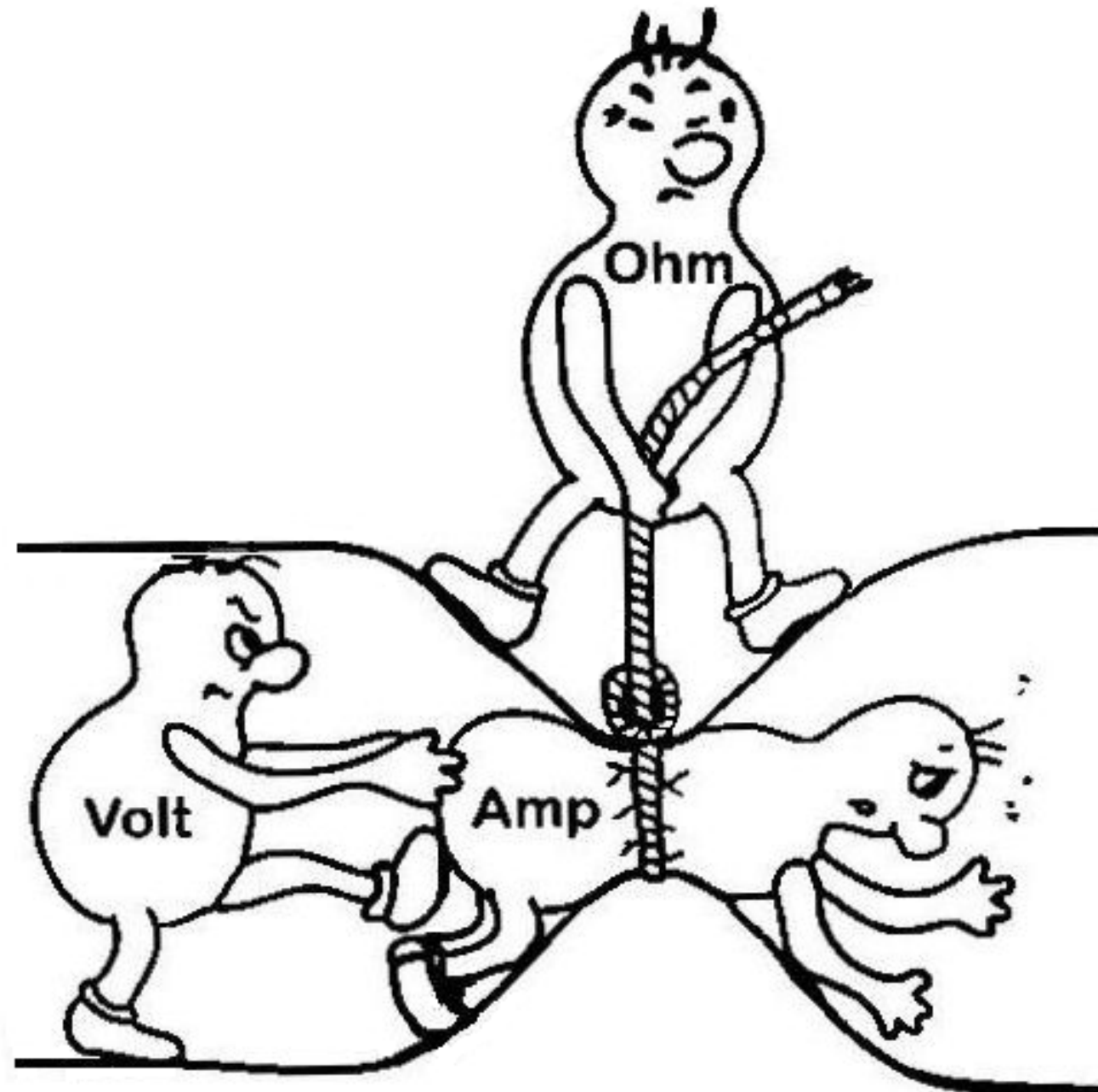
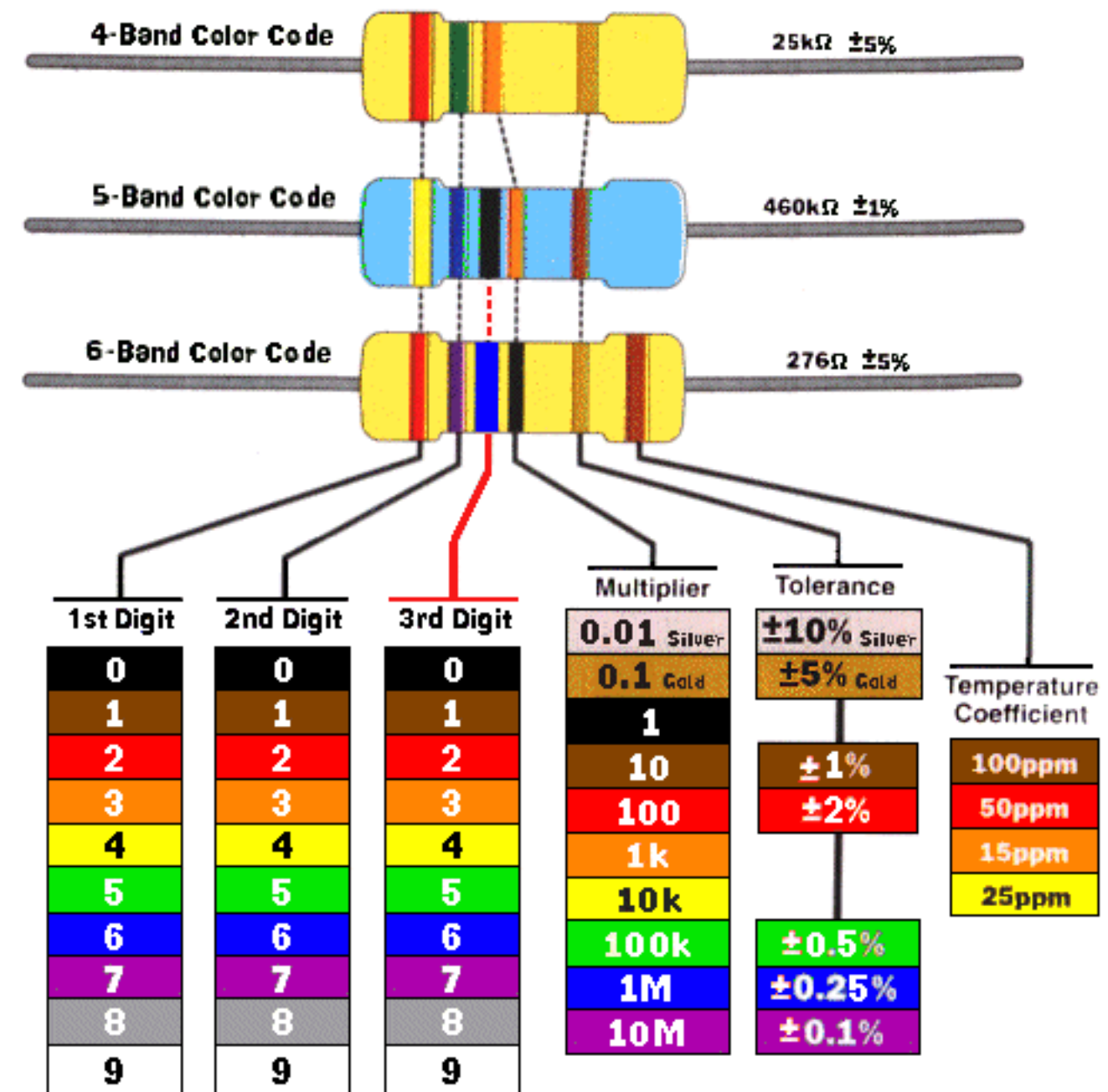


image source: <http://www.sengpielaudio.com/Rechner-ohmschesgesetz.htm>

# Components - Resistor

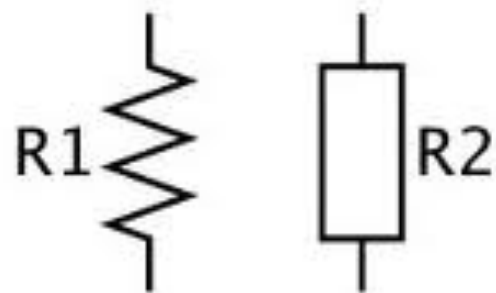



# Components - Buttons

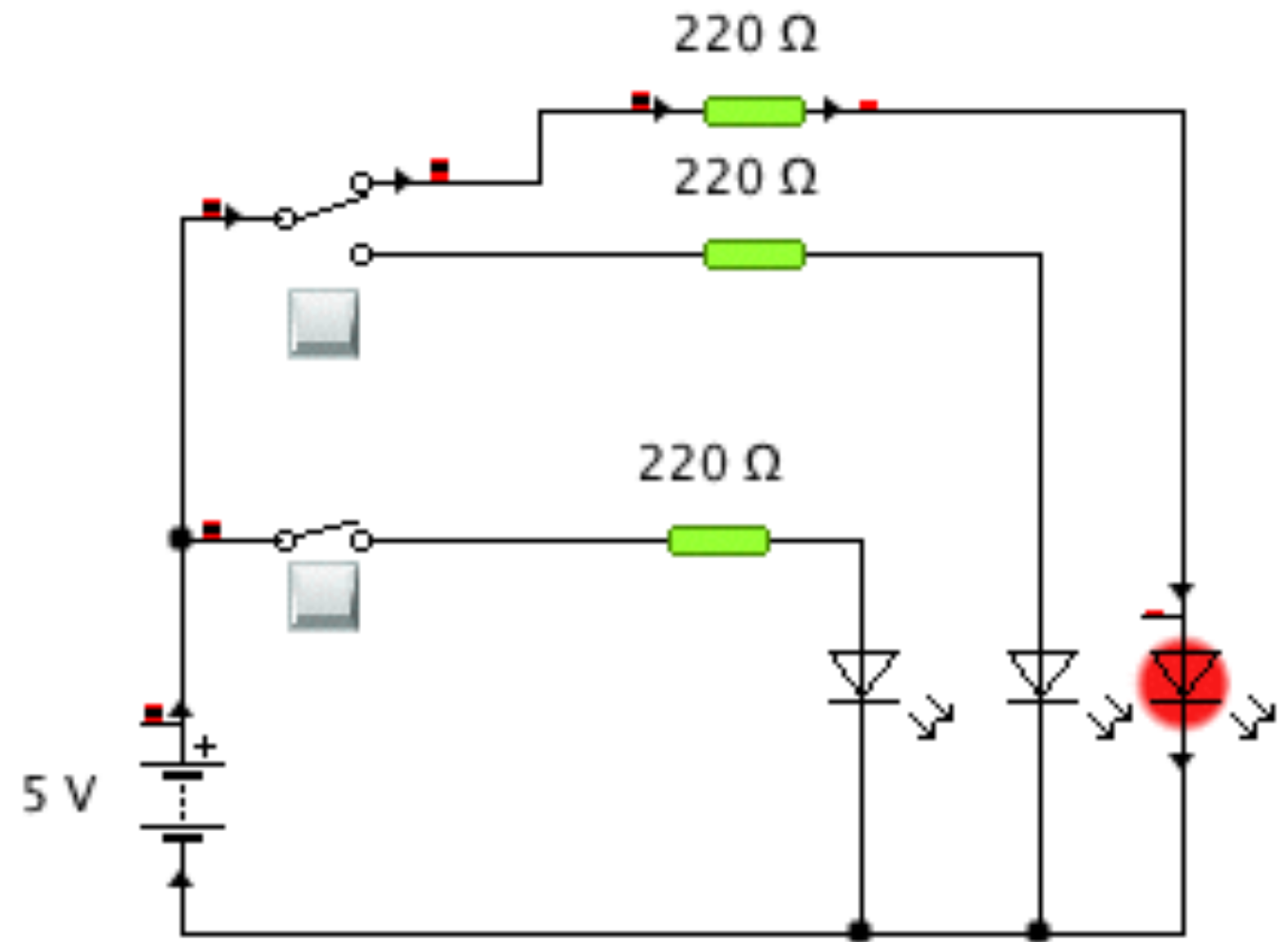



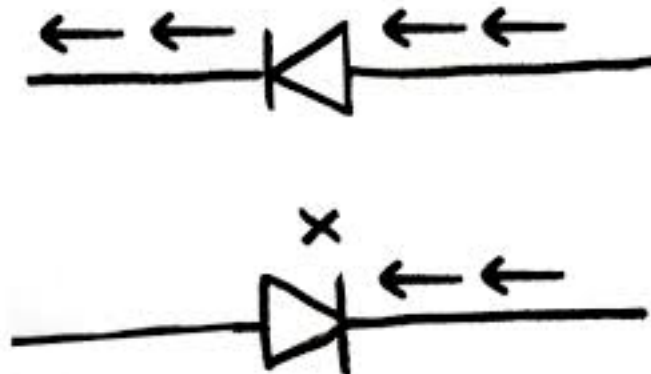
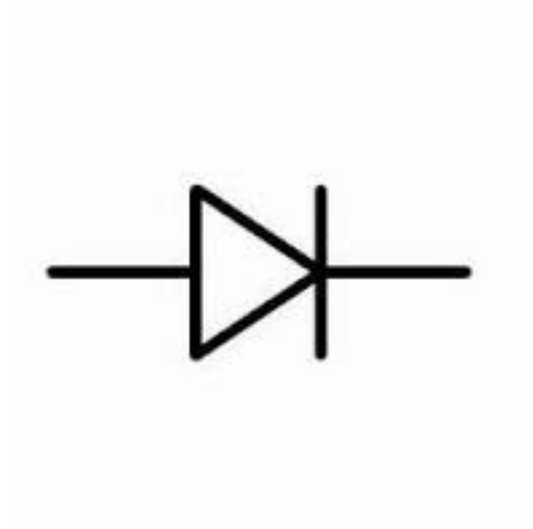
# Components - Diodes

- allows current to pass in one direction only
- often used to decouple the effect of one component from another
- special case: LED = light emitting diode



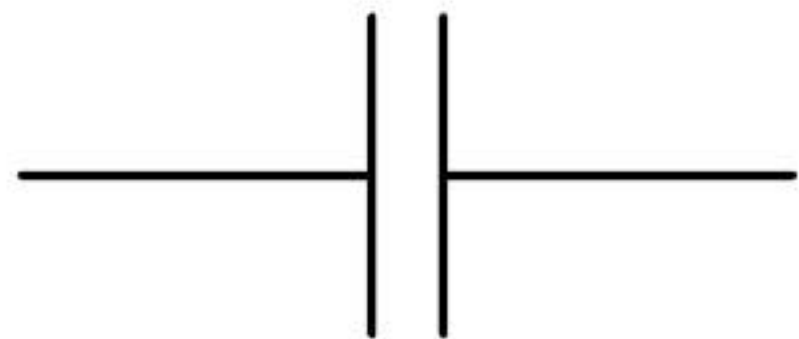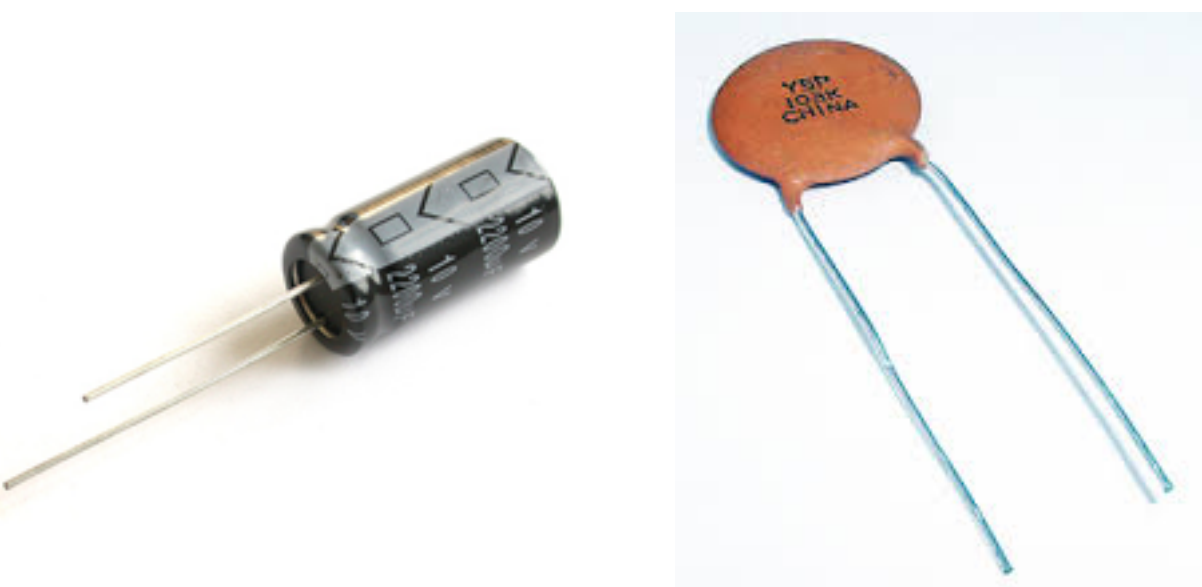
# Components - Capacitor

simplification: capacitors are like batteries  
work in completely different ways, but both can store  
electrical energy



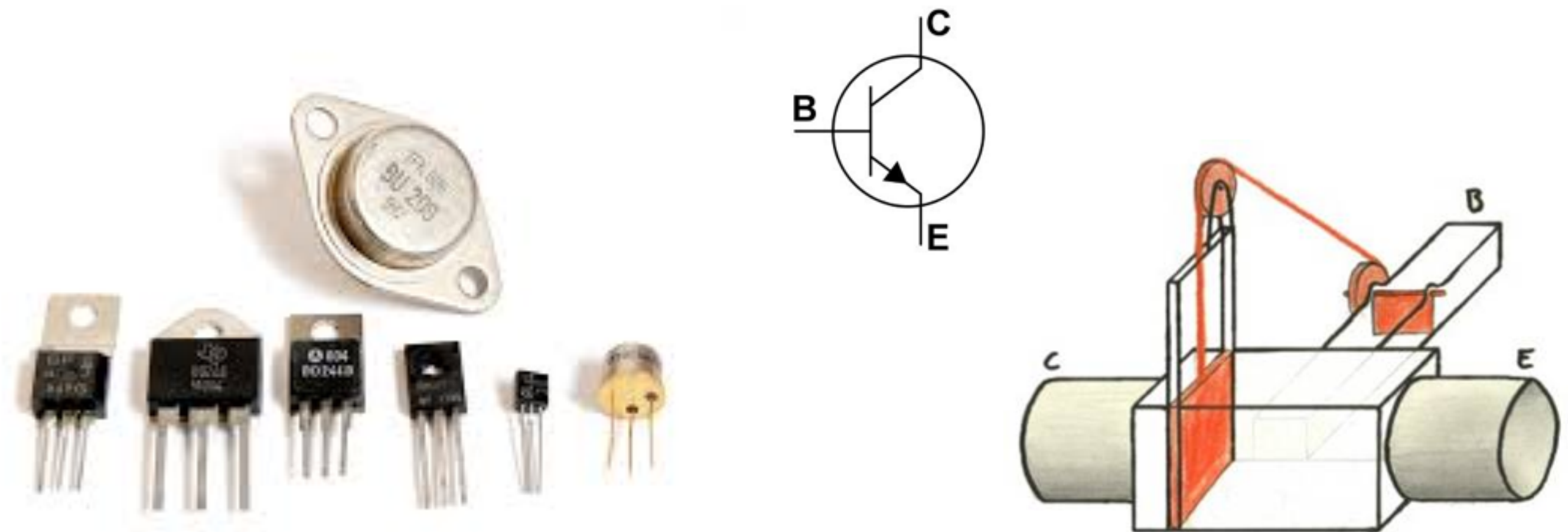
# Components - Transistor


simplification: electronic version of a switch



# Measure Voltage

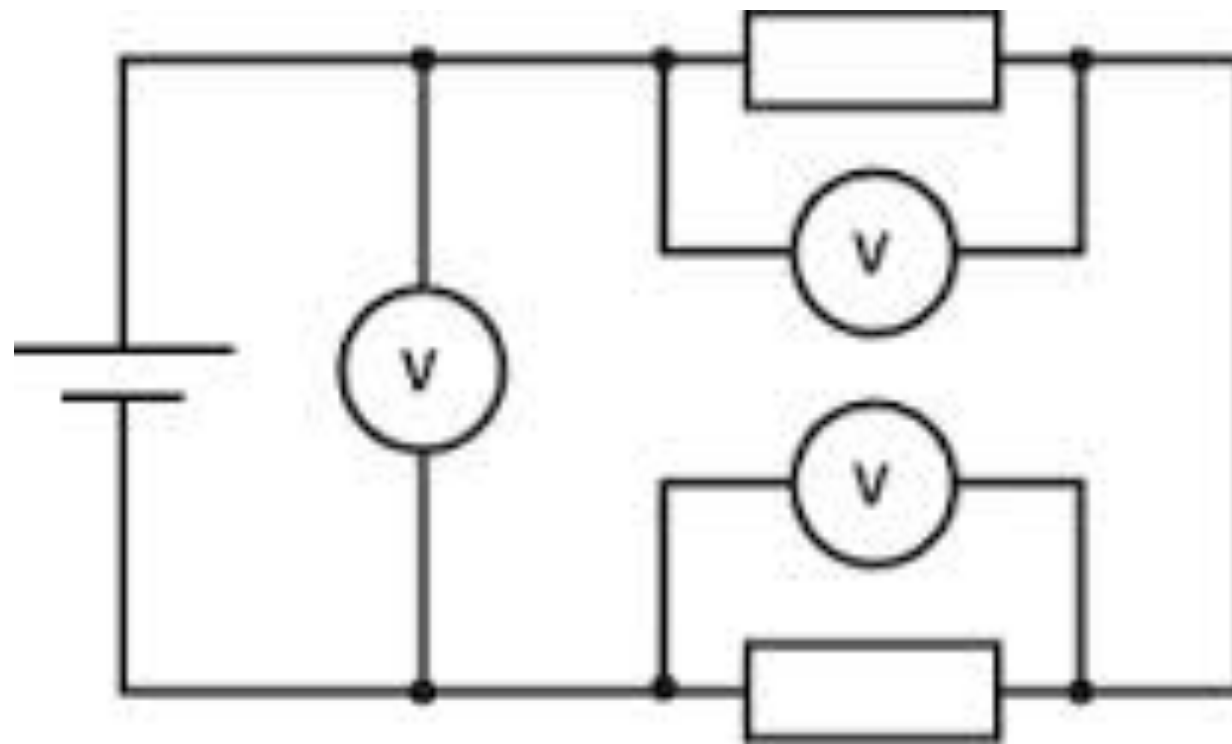

# Measuring Current

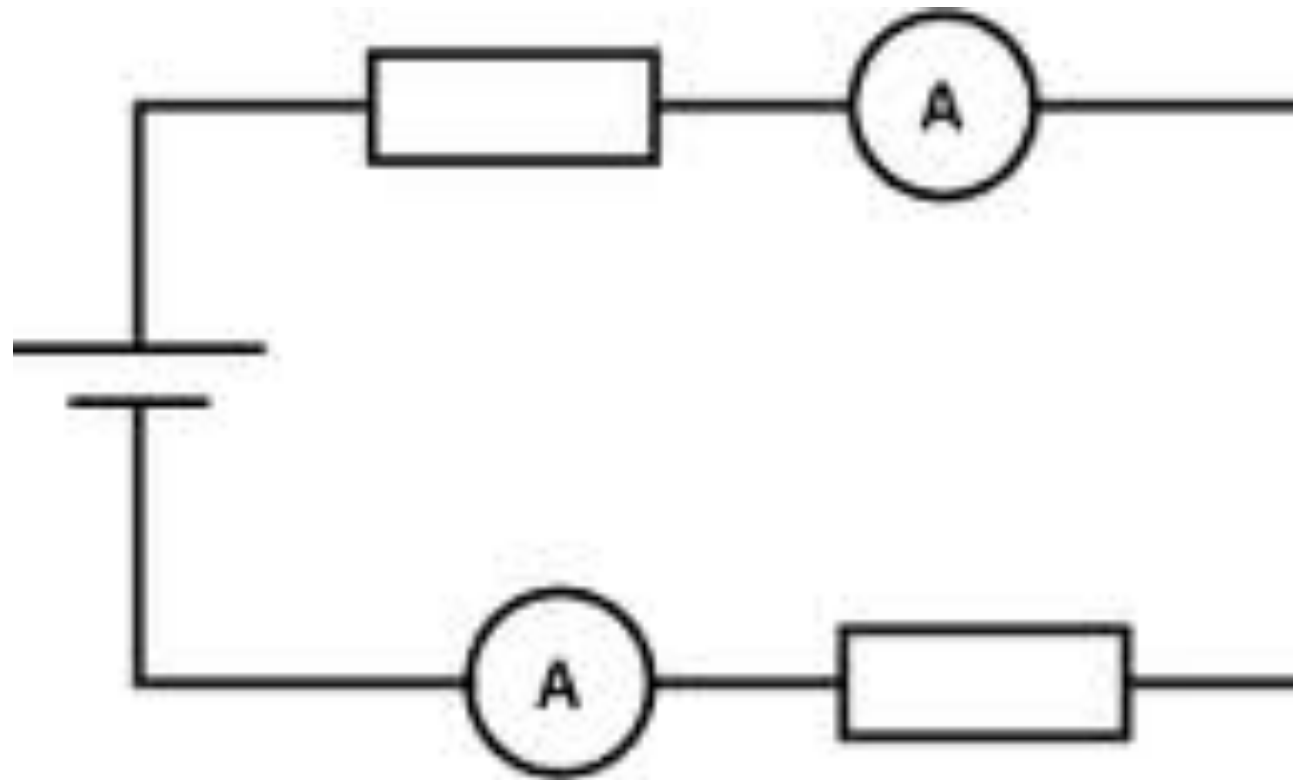

# Arduino Circuit

